

# Electronic Devices

**Course Teacher**  
**Niloy Goswami**

**Prepared By**  
**Dr. Md. Kabiruzzaman**


Reference book:

**Electronic Devices and Circuit Theory (Chapter-2)**

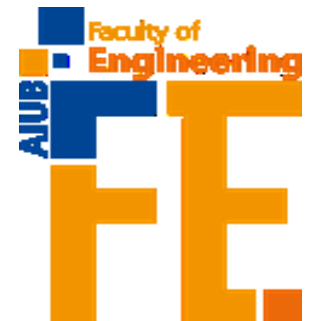**Robert L. Boylestad and L. Nashelsky , (11<sup>th</sup> Edition)**



*Department of Electrical and Electronics Engineering*  
*American International University-Bangladesh(AIUB)*




# Objectives

- ☆ Understand the concept of load-line analysis and how it is applied to diode networks.
- ☆ Become familiar with the use of equivalent circuits to analyze series, parallel, and series-parallel diode networks.

# LOAD-LINE ANALYSIS


- The load line plots all possible combinations of diode current ( $I_D$ ) and voltage ( $V_D$ ) for a given circuit.
- The maximum  $I_D$  equals  $E/R$ , and the maximum  $V_D$  equals  $E$ .
- The point where the load line and the characteristic curve intersect is the Q-point, which identifies  $I_D$  and  $V_D$  for a particular diode in a given circuit.

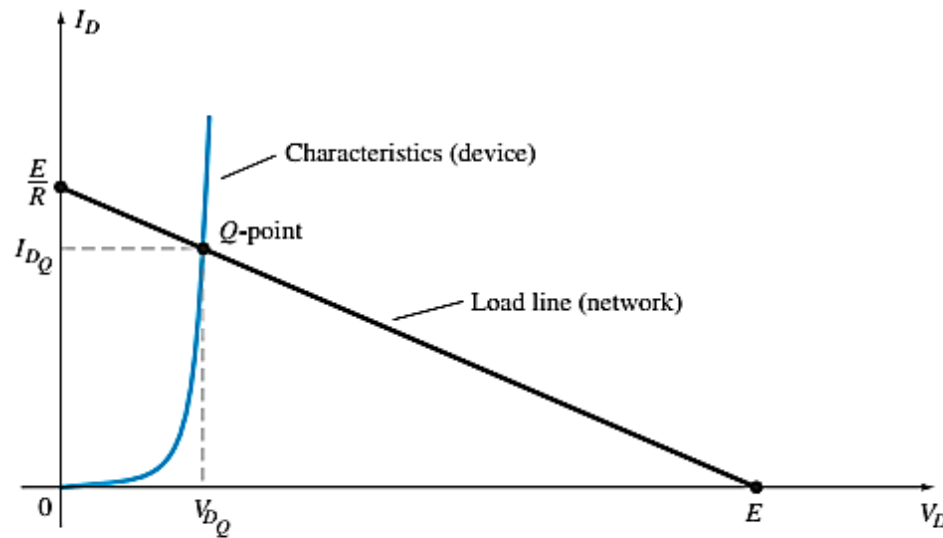

**FIG. 2.2**

*Drawing the load line and finding the point of operation.*

# LOAD-LINE ANALYSIS

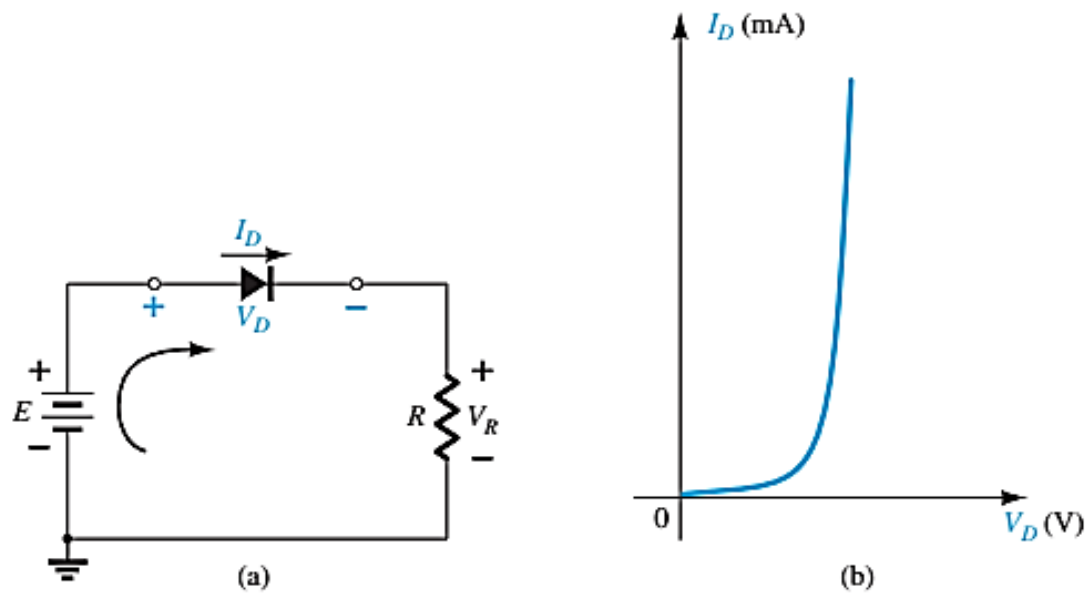

**FIG. 2.1**

*Series diode configuration: (a) circuit; (b) characteristics.*

$$+E - V_D - V_R = 0$$

$$E = V_D + I_D R$$

$$\begin{aligned} E &= V_D + I_D R \\ &= 0 \text{ V} + I_D R \end{aligned}$$

$$I_D = \frac{E}{R} \bigg|_{V_D=0 \text{ V}}$$

$$\begin{aligned} E &= V_D + I_D R \\ &= V_D + (0 \text{ A}) R \end{aligned}$$

$$V_D = E \big|_{I_D=0 \text{ A}}$$

# LOAD-LINE ANALYSIS

**EXAMPLE 2.1** For the series diode configuration of Fig. 2.3a, employing the diode characteristics of Fig. 2.3b, determine:

- $V_{DQ}$  and  $I_{DQ}$ .
- $V_R$ .

**Solution:**

a. Eq. (2.2): 
$$I_D = \frac{E}{R} \bigg|_{V_D=0\text{ V}} = \frac{10\text{ V}}{0.5\text{ k}\Omega} = 20\text{ mA}$$


Eq. (2.3): 
$$V_D = E \big|_{I_D=0\text{ A}} = 10\text{ V}$$

The resulting load line appears in Fig. 2.4. The intersection between the load line and the characteristic curve defines the  $Q$ -point as

$$V_{DQ} \cong 0.78\text{ V}$$

$$I_{DQ} \cong 18.5\text{ mA}$$


b. 
$$V_R = E - V_D = 10\text{ V} - 0.78\text{ V} = 9.22\text{ V}$$

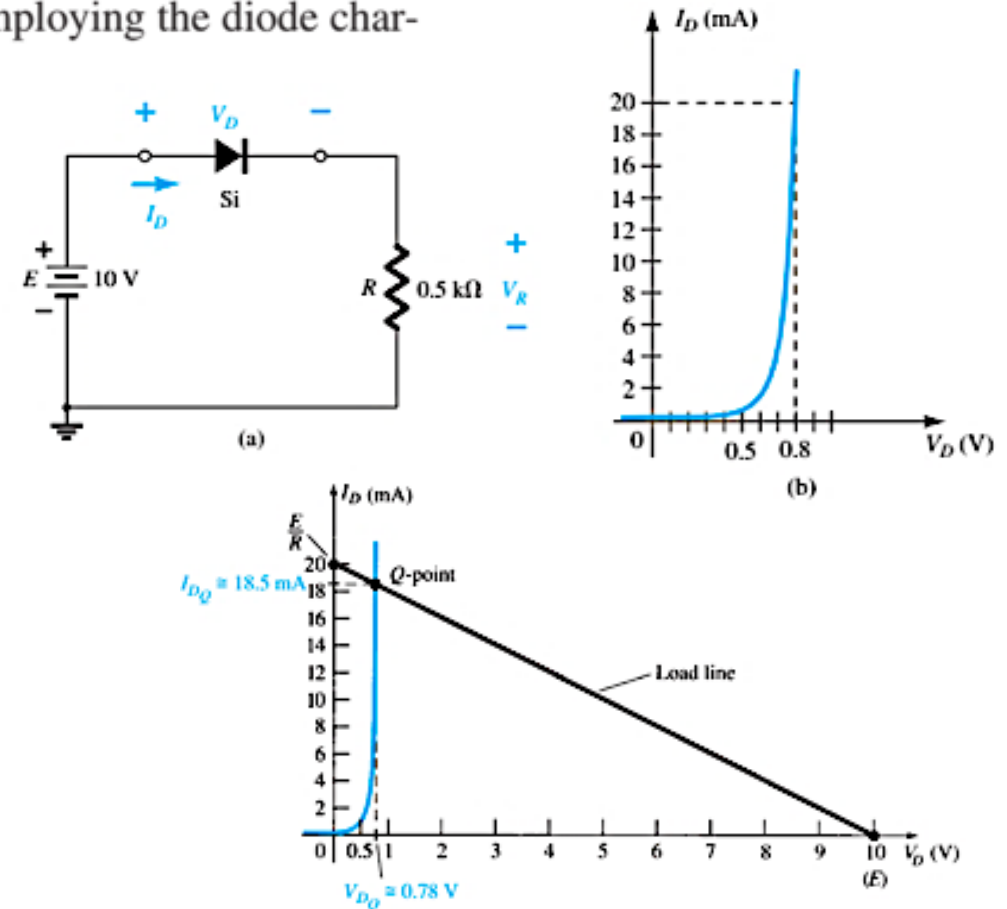

**FIG. 2.4**  
Solution to Example 2.1.

# LOAD-LINE ANALYSIS

$$R_D = \frac{V_{DQ}}{I_{DQ}} = \frac{0.78 \text{ V}}{18.5 \text{ mA}} = 42.16 \Omega$$

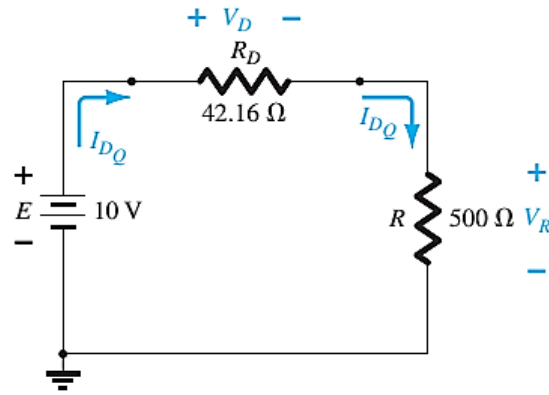


**FIG. 2.5**

Network equivalent to Fig. 2.4.

$$I_D = \frac{E}{R_D + R} = \frac{10 \text{ V}}{42.16 \Omega + 500 \Omega} = \frac{10 \text{ V}}{542.16 \Omega} \cong 18.5 \text{ mA}$$

$$V_R = \frac{RE}{R_D + R} = \frac{(500 \Omega)(10 \text{ V})}{42.16 \Omega + 500 \Omega} = 9.22 \text{ V}$$

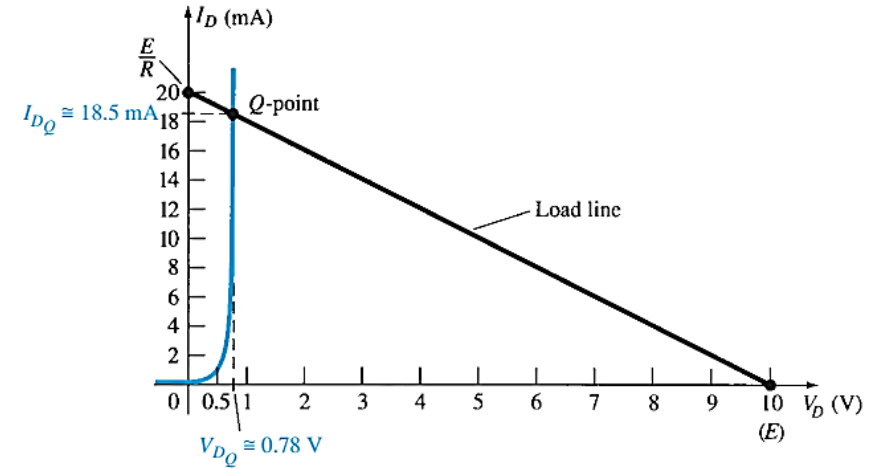


**FIG. 2.4**

Solution to Example 2.1.


# SERIES DIODE CONFIGURATIONS

**TABLE 2.1**

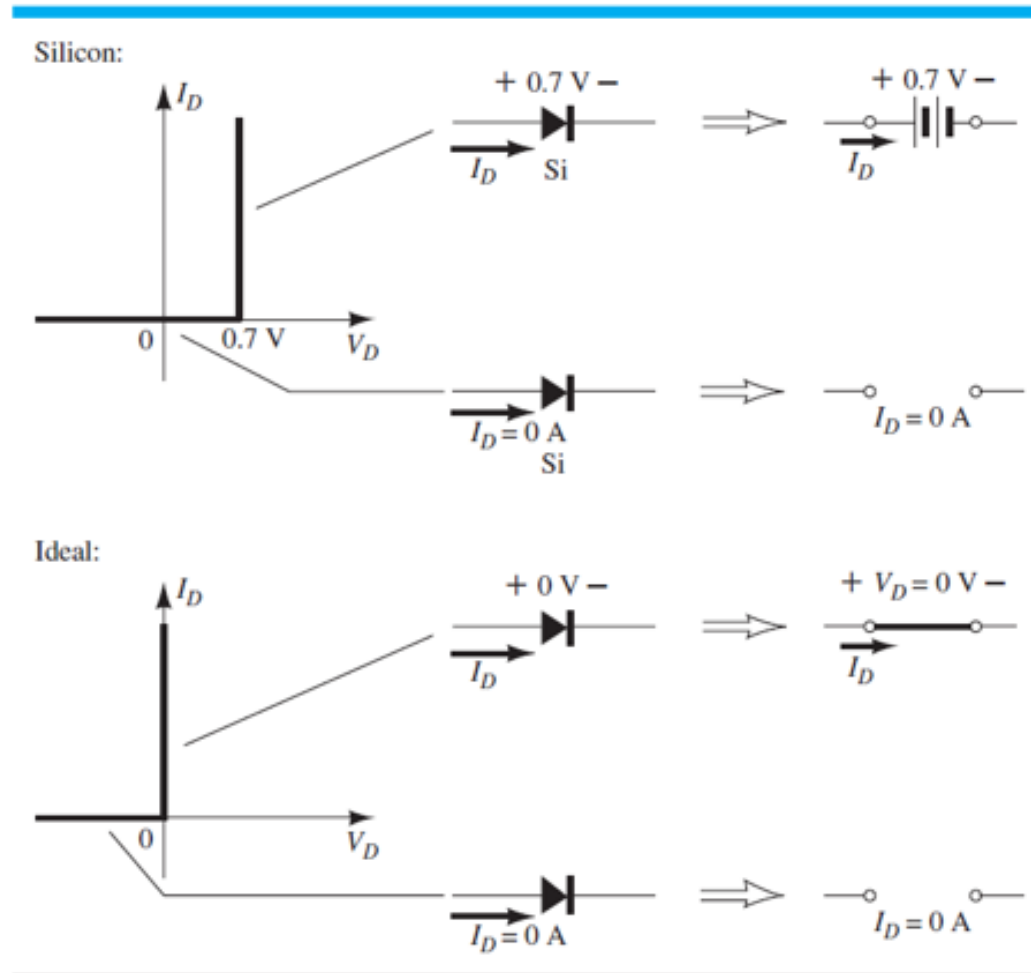
*Approximate and Ideal Semiconductor Diode Models.*



# SERIES DIODE CONFIGURATIONS

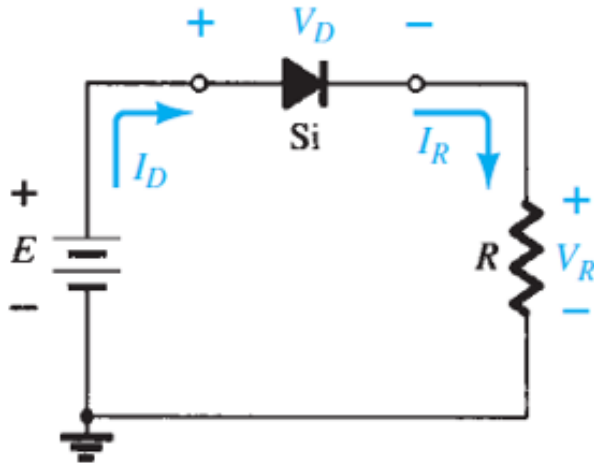


**FIG. 2.8**  
*Series diode configuration.*

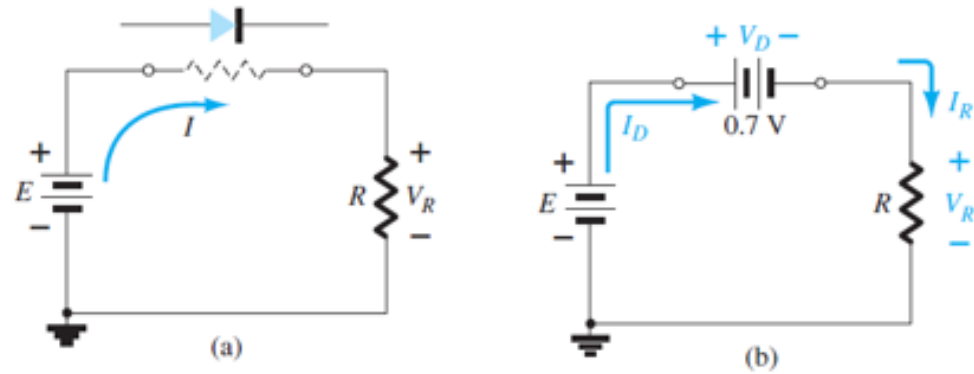

**FIG. 2.9**  
(a) *Determining the state of the diode of Fig. 2.8; (b) substituting the equivalent model for the “on” diode of Fig. 2.9a.*




# SERIES DIODE CONFIGURATIONS

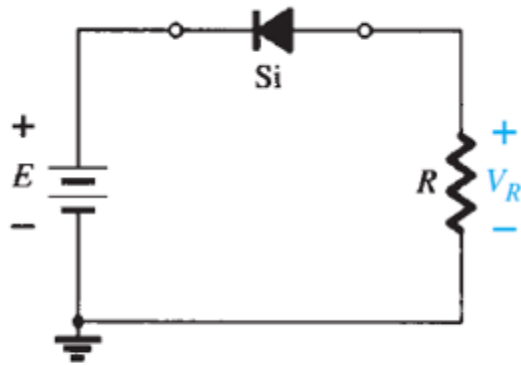


**FIG. 2.10**

*Reversing the diode of Fig. 2.8.*

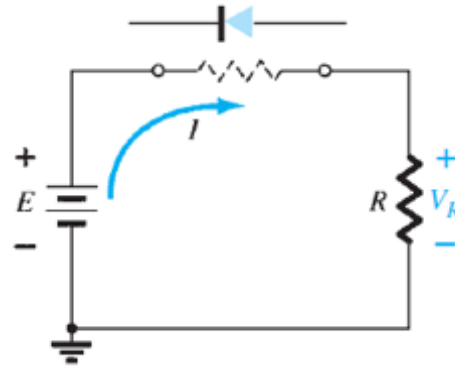

**FIG. 2.11**

*Determining the state of the diode of Fig. 2.10.*

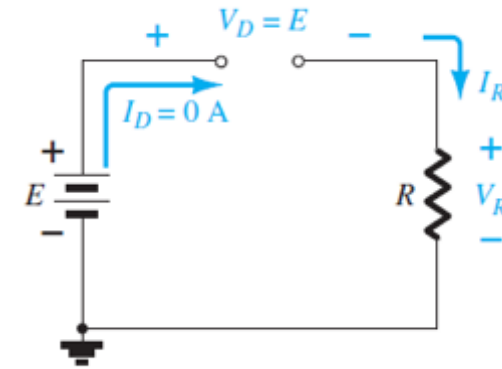

**FIG. 2.12**

*Substituting the equivalent model for the “off” diode of Fig. 2.10.*


# SERIES DIODE CONFIGURATIONS

**EXAMPLE 2.4** For the series diode configuration of Fig. 2.13, determine  $V_D$ ,  $V_R$ , and  $I_D$ .

$$V_D = 0.7 \text{ V}$$

$$V_R = E - V_D = 8 \text{ V} - 0.7 \text{ V} = 7.3 \text{ V}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{7.3 \text{ V}}{2.2 \text{ k}\Omega} \cong 3.32 \text{ mA}$$

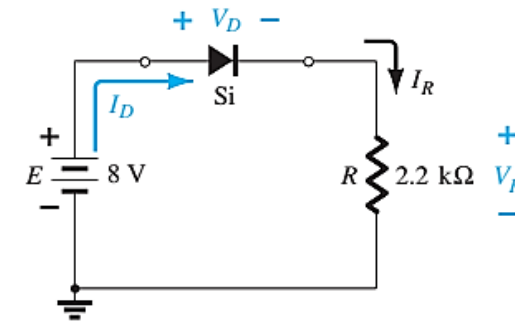


**FIG. 2.13**

*Circuit for Example 2.4.*

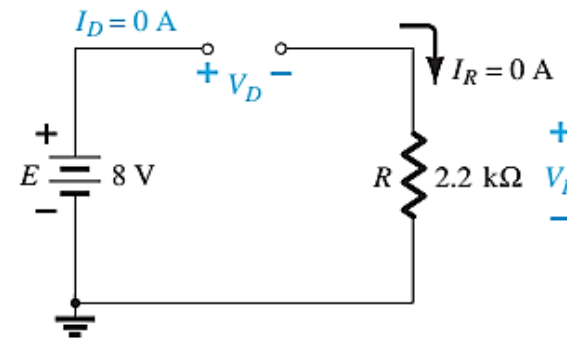**EXAMPLE 2.5** Repeat Example 2.4 with the diode reversed.

$$E - V_D - V_R = 0$$

$$V_D = E - V_R = E - 0 = E = 8 \text{ V}$$




# SERIES DIODE CONFIGURATIONS

For the series diode configuration of Fig. 2.16, determine  $V_D$ ,  $V_R$ , and  $I_D$ .

$$I_D = 0 \text{ A}$$


$$V_R = I_R R = I_D R = (0 \text{ A}) 1.2 \text{ k}\Omega = 0 \text{ V}$$

$$V_D = E = 0.5 \text{ V}$$

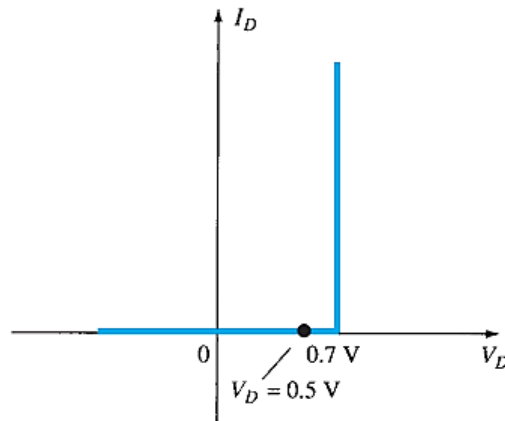


**FIG. 2.17**

Operating point with  $E = 0.5 \text{ V}$ .

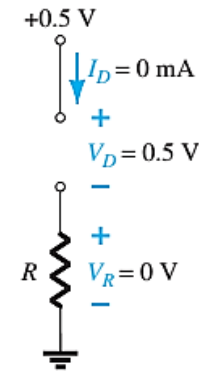

**FIG. 2.18**

Determining  $I_D$ ,  $V_R$ , and  $V_D$  for the circuit of Fig. 2.16.

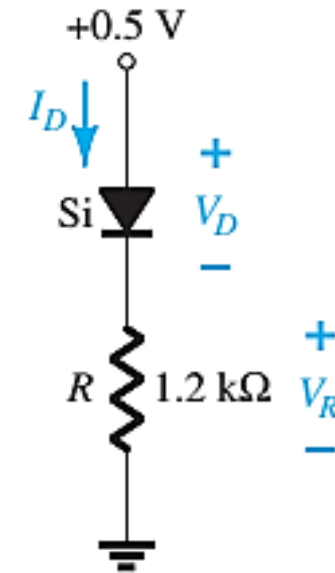


**FIG. 2.16**

Series diode circuit for Example 2.6.


# SERIES DIODE CONFIGURATIONS

**EXAMPLE 2.7** Determine  $V_o$  and  $I_D$  for the series circuit of Fig. 2.19.

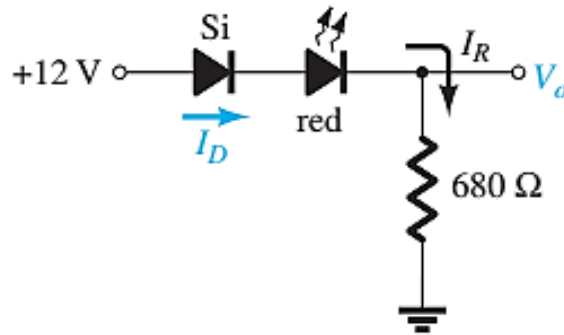

**FIG. 2.19**

*Circuit for Example 2.7.*

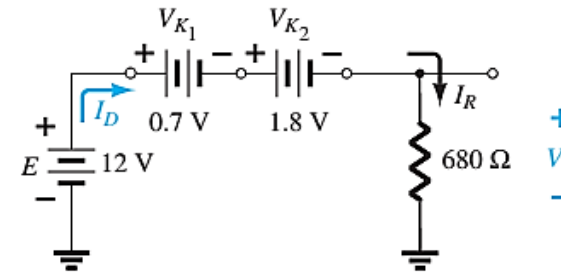

**FIG. 2.20**

*Determining the unknown quantities for Example 2.7.*


$$E = 12 \text{ V} > (0.7 \text{ V} + 1.8 \text{ V [Table 1.8]}) = 2.5 \text{ V}.$$

$$V_o = E - V_{K1} - V_{K2} = 12 \text{ V} - 2.5 \text{ V} = \mathbf{9.5 \text{ V}}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{V_o}{R} = \frac{9.5 \text{ V}}{680 \Omega} = \mathbf{13.97 \text{ mA}}$$

# SERIES DIODE CONFIGURATIONS

**EXAMPLE 2.8** Determine  $I_D$ ,  $V_{D_2}$ , and  $V_o$  for the circuit of Fig. 2.21.

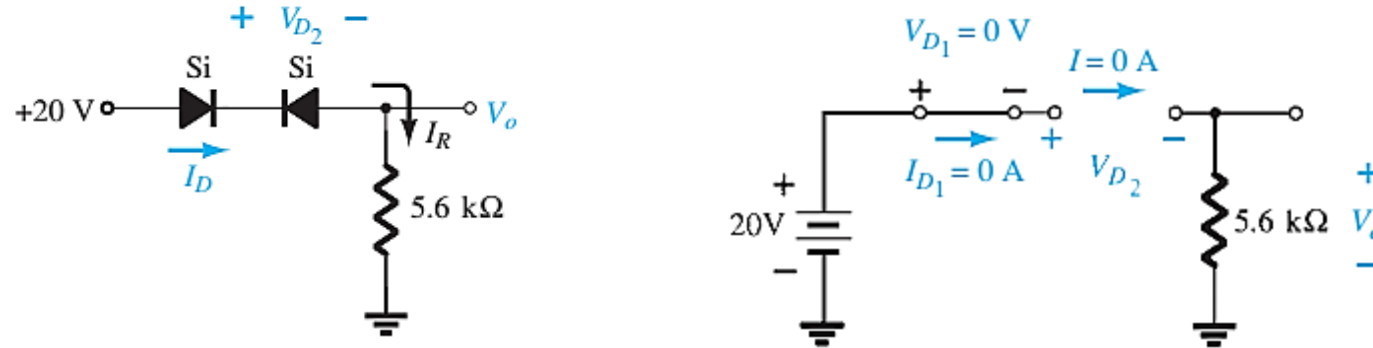

**FIG. 2.21**

*Circuit for Example 2.8.*

$$I_D = 0 \text{ A}$$

$$V_o = I_R R = I_D R = (0 \text{ A})R = 0 \text{ V}$$

$$V_{D_2} = V_{\text{open circuit}} = E = 20 \text{ V}$$

Applying Kirchhoff's voltage law in a clockwise direction gives


$$E - V_{D_1} - V_{D_2} - V_o = 0$$

and

$$\begin{aligned} V_{D_2} &= E - V_{D_1} - V_o = 20 \text{ V} - 0 - 0 \\ &= 20 \text{ V} \end{aligned}$$

# SERIES DIODE CONFIGURATIONS

**EXAMPLE 2.9** Determine  $I$ ,  $V_1$ ,  $V_2$ , and  $V_o$  for the series dc configuration of Fig. 2.25.

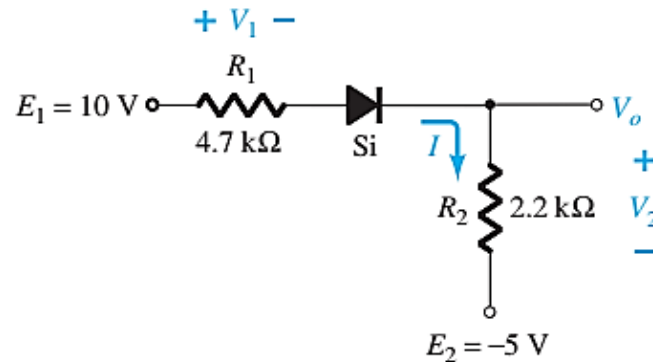


**FIG. 2.25**

Circuit for Example 2.9.

$$I = \frac{E_1 + E_2 - V_D}{R_1 + R_2} = \frac{10\text{ V} + 5\text{ V} - 0.7\text{ V}}{4.7\text{ k}\Omega + 2.2\text{ k}\Omega} = \frac{14.3\text{ V}}{6.9\text{ k}\Omega} \cong 2.07\text{ mA}$$

$$V_1 = IR_1 = (2.07\text{ mA})(4.7\text{ k}\Omega) = 9.73\text{ V}$$

$$V_2 = IR_2 = (2.07\text{ mA})(2.2\text{ k}\Omega) = 4.55\text{ V}$$

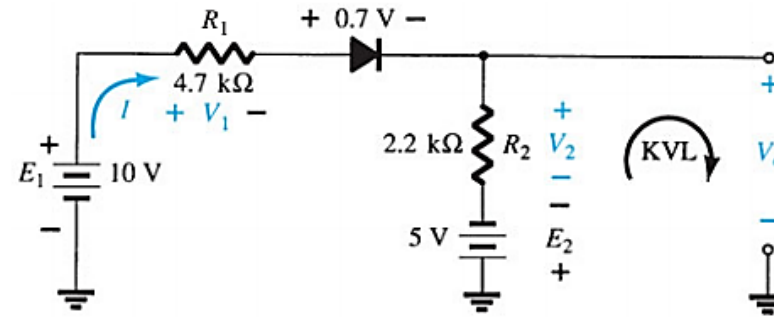

**FIG. 2.27**

Determining the unknown quantities for the network of Fig. 2.25. KVL, Kirchhoff voltage loop.


Applying KVL,

$$-E_2 + V_2 - V_o = 0$$

$$V_o = V_2 - E_2 = 4.55\text{ V} - 5\text{ V} = -0.45\text{ V}$$


# SERIES-PARALLEL CONFIGURATIONS

**EXAMPLE 2.10** Determine  $V_o$ ,  $I_1$ ,  $I_{D_1}$ , and  $I_{D_2}$  for the parallel diode configuration of Fig. 2.28.

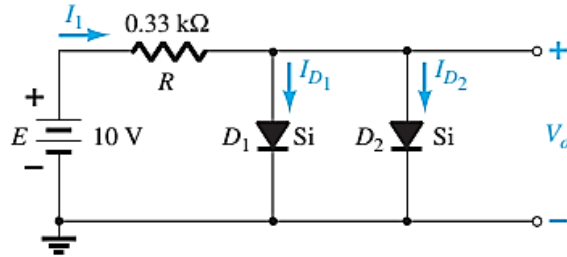

**FIG. 2.28**

*Network for Example 2.10.*

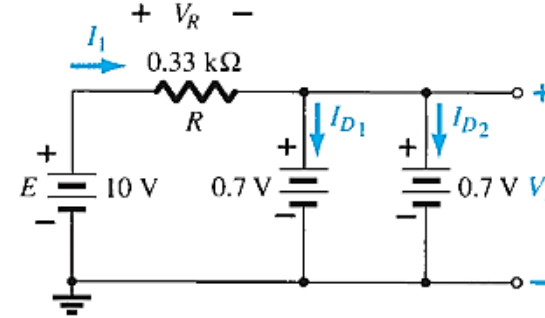

**FIG. 2.29**

*Determining the unknown quantities for the network of Example 2.10.*

$$V_o = 0.7 \text{ V}$$


$$I_1 = \frac{V_R}{R} = \frac{E - V_D}{R} = \frac{10 \text{ V} - 0.7 \text{ V}}{0.33 \text{ k}\Omega} = 28.18 \text{ mA}$$

$$I_{D_1} = I_{D_2} = \frac{I_1}{2} = \frac{28.18 \text{ mA}}{2} = 14.09 \text{ mA}$$


□ **See Example 2.11**

# SERIES-PARALLEL CONFIGURATIONS

**EXAMPLE 2.12** Determine the voltage  $V_o$  for the network of Fig. 2.35.

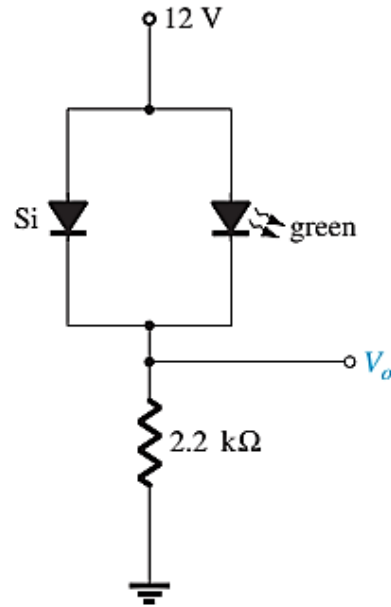

**FIG. 2.35**  
Network for Example 2.12.

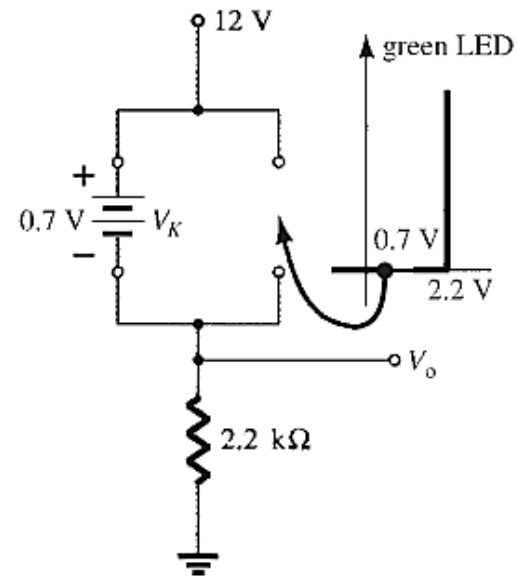


**FIG. 2.36**  
Determining  $V_o$  for the network of Fig. 2.35.

$$V_o = 12 \text{ V} - 0.7 \text{ V} = 11.3 \text{ V}$$




# SERIES-PARALLEL CONFIGURATIONS

**EXAMPLE 2.13** Determine the currents  $I_1$ ,  $I_2$ , and  $I_{D_2}$  for the network of Fig. 2.37.

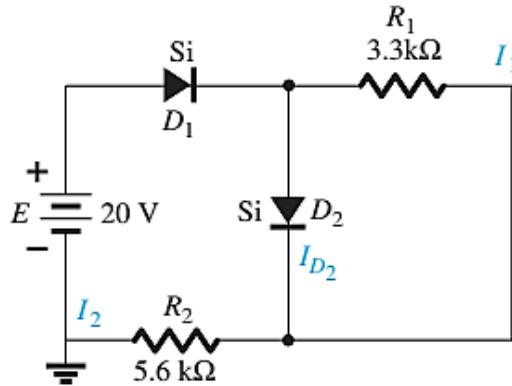

**FIG. 2.37**

Network for Example 2.13.

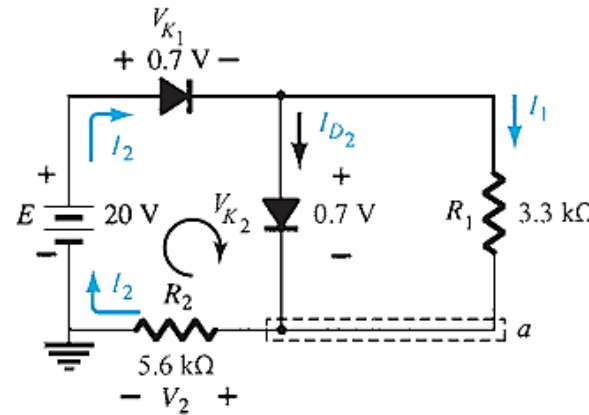

**FIG. 2.38**

Determining the unknown quantities for Example 2.13.

$$I_1 = \frac{V_{K_2}}{R_1} = \frac{0.7 \text{ V}}{3.3 \text{ k}\Omega} = \mathbf{0.212 \text{ mA}}$$

$$\begin{aligned} -V_2 + E - V_{K_1} - V_{K_2} &= 0 \\ V_2 = E - V_{K_1} - V_{K_2} &= 20 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V} = \mathbf{18.6 \text{ V}} \\ I_2 = \frac{V_2}{R_2} &= \frac{18.6 \text{ V}}{5.6 \text{ k}\Omega} = \mathbf{3.32 \text{ mA}} \end{aligned}$$

$$\begin{aligned} I_{D_2} + I_1 &= I_2 \\ I_{D_2} = I_2 - I_1 &= 3.32 \text{ mA} - 0.212 \text{ mA} \cong \mathbf{3.11 \text{ mA}} \end{aligned}$$

□ **See Example 2.14 and 2.15**

# Thank You